

Design of Digital Circuits

Summary

April 18, 2020

Chapter 1

From Zero to One

1.1 Managing Complexity

Abstraction: The levels of abstraction for an electronic computer:

- **physics:** The motion of electrons
- **electronic devices:** Transistors which have connection points (terminals) and can be modeled by the relationship between voltage and current as measured at each terminal.
- **analog circuits:** Devices which are assembled to create components such as amplifiers. They input and output a continuous range of voltages
- **Digital circuits:** e.g logic gates restrict the voltages to discrete ranges which we use to indicate 0 and 1.
- **Microarchitecture:** Links the logic and architecture levels of abstraction. Microarchitecture involves combining logic elements to execute the instructions defined by the architecture-
- **Architecture:** Describes the computer from the programmers perspective. A particular architecture can be implemented by one of many different microarchitectures.
- **Operating system:** Handles low-level details such as accessing a hard drive or managing memory.
- **Application software:** Uses the facilities provided by the operating system to solve a problem for the user.

Discipline: the act of intentionally restricting your design choices so that you can work more productively at a higher level of abstraction.

The Three- Y's:

- **Hierarchy:** involves dividing a system into modules then further subdividing each of these modules until the pieces are easy to understand
- **Modularity:** states that the modules have well-defined functions and interfaces so that they connect together easily without unanticipated side effects
- **Regularity:** seeks uniformity among the modules. Common modules are reused many times, reducing the number of distinct modules that must be designed

1.2 Digital Abstraction:

Discrete-valued variables: Variables with a finite number of distinct values. Most electronic computers use a binary representation in which a high voltage indicates a 1 and a low voltage indicates a 0. The amount of information D in a discrete valued variable with N distinct states is measured in units of bits as:

$$D = \log_2 N \text{ bits}$$

hence a binary variable conveys $\log_2 2 = 1$ bit of information

1.3 Number Systems


Binary Numbers: Bits represent one of two values 0 or 1 and are joined together to form binary numbers. Each column of a binary number has twice the weight of the previous column, hence they are base 2 (the base is denoted as subscript e.g 10110_2).

Hexadecimal Numbers: groups of four bits i.e base 16. Hexadecimal numbers use the digits 0 to 9 along with the letters A to F

| Hexadecimal Digit | Decimal Equivalent | Binary Equivalent |
|-------------------|--------------------|-------------------|
| 0 | 0 | 0000 |
| 1 | 1 | 0001 |
| 2 | 2 | 0010 |
| 3 | 3 | 0011 |
| 4 | 4 | 0100 |
| 5 | 5 | 0101 |
| 6 | 6 | 0110 |
| 7 | 7 | 0111 |
| 8 | 8 | 1000 |
| 9 | 9 | 1001 |
| A | 10 | 1010 |
| B | 11 | 1011 |
| C | 12 | 1100 |
| D | 13 | 1101 |
| E | 14 | 1110 |
| F | 15 | 1111 |

Bytes, Nibbles, etc: A group of eight bits is called a byte. The size of objects stored in computer memories is measured in bytes rather than bits. A group of four bits, is called a nibble i.e one hexadecimal digit stores one nibble. Microprocessors handle data in chunks called words which the size of depends on the architecture of the microprocessor (64 bit processors indicate that they operate on 64-bit words)

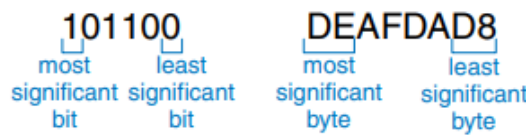Most/Least significant bit (lsb/msb): Within a group of bits in the 1's column is called the lsb and the bit at the other end is called the msb



Estimating Powers of Two:

- $2^{10} \approx 10^3$
- $2^{20} \approx 10^6$
- $2^{30} \approx 10^9$

Binary Addition

:

Figure 1.8 Addition examples showing carries: (a) decimal (b) binary

$$\begin{array}{r}
 \begin{array}{c}
 11 \\
 4277 \\
 + 5499 \\
 \hline
 9776
 \end{array}
 \quad \leftarrow \text{carries} \rightarrow \quad
 \begin{array}{c}
 11 \\
 1011 \\
 + 0011 \\
 \hline
 1110
 \end{array}
 \end{array}$$

(a) (b)

Signed Binary Numbers: The two most widely employed systems to represent signed binary numbers are:

- **Sign/magnitude:** The msb is used as the sign and the remaining N-1 bits is the absolute value. 0 indicates positive and 1 indicates negative. Ordinary binary addition does not work for sign/magnitude numbers. (0 has two representations)
- **Two's complement:** Identical to unsigned binary numbers except that the most significant bit position has a weight of -2^{N-1} instead of 2^{N-1} . Zero has a single representation and ordinary addition works. The sing of a two's complement number is reversed in a process called taking the two's complement. The process consists of inverting all of the bits in the number, then adding 1 to the least significant bit position. When addint N-bit numbers, the carry out of the Nth bit is discarded. Subtraction is performed by taking the two's complement of the second number, then adding. The range of an N-bit twos complement number spans $[-2^{N-1}, 2^{N-1} - 1]$

1.4 Logic Gates

Logic Gates: are simple digital circuits that take one or more binary inputs and produce a binary output. Logic gates are drawn with a symbol showing the input and the output. Inputs are drawn on the left or top and recieve a letter near the beginning of the alphabet and the outputs on the right or bottom and recieve the letter Y.

Truth table: Lists the inputs on the left and the corresponding output on the right. One row is designated for each possible combination of inputs.

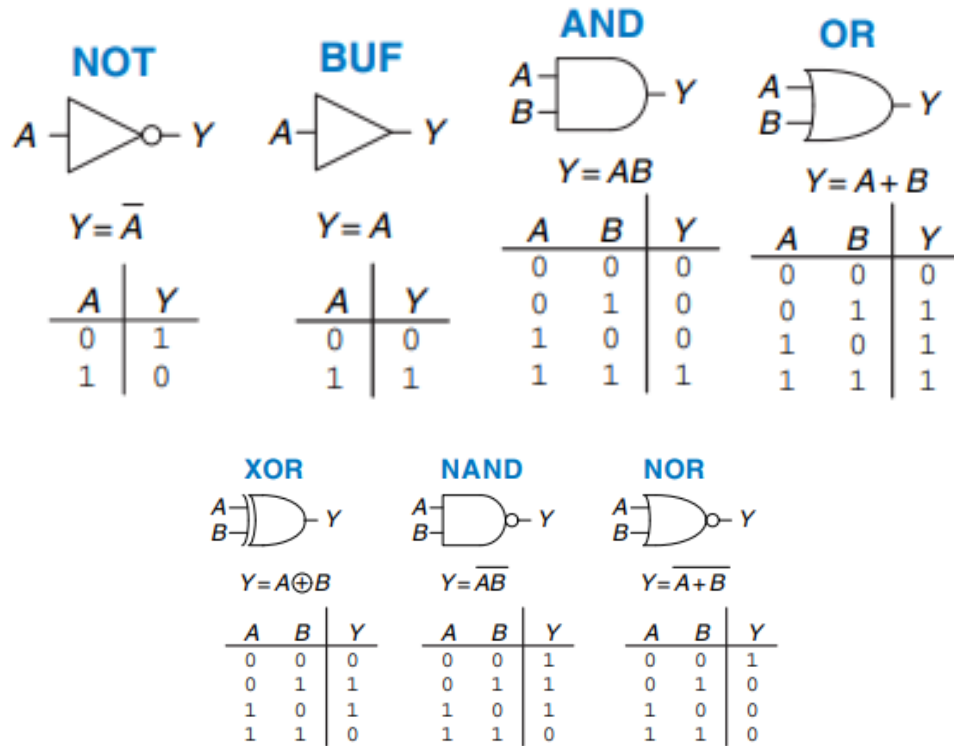


Figure 1.1: Common Gates


Bubble: circle on the output of a logic gate indicating an inversion.

N-input XOR: Produces true when an odd number of inputs are TRUE.

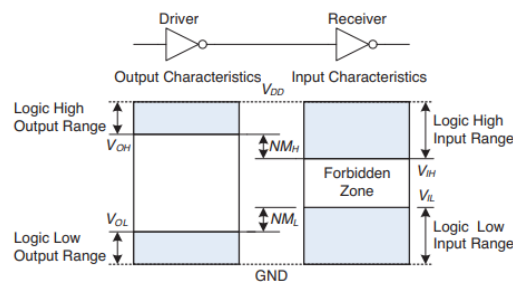1.5 Beneath the digital Abstraction

Supply Voltage: The lowest voltage in a system is called ground or GND (0V). The highest voltage comes from the power supply and is usually called V_{DD} .

Logic Levels and Noise Margins: used to map continuous variables onto discrete binary variables.



The driver produces a LOW(0) output in the range of 0 to V_{OL} or a HIGH(1) in the range of V_{OH} to V_{DD} . If the receiver gets an input in the range of 0 to V_{IL} it will consider the input to be LOW, if it gets an input in the range of V_{IH} to V_{DD} it will consider the input to be HIGH. If the receiver's input falls into the forbidden zone the behaviour of the gate is unpredictable. $V_{OH}, V_{OL}, V_{IH}, V_{IL}$ are called the output and input high and low logic levels. The noise margin is the amount of noise that could be added to a worst-case output such that the signal can still be interpreted as a valid input.

$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

DC transfer characteristics: of a gate describes the output voltage as a function of the input voltage when the input is changed slowly enough that the output can keep up. A reasonable place to choose logic levels is where the slope of the transfer characteristics $\frac{dV(Y)}{dV(A)} = -1$. These two points are called **unity gain points**. This usually maximizes the noise margins.

Static Discipline: Given logically valid inputs, every circuit element will produce logically valid outputs. The choice of V_{DD} and logic levels is arbitrary, but all gates that communicate must have compatible logic levels. Gates are grouped into logic families such that all gates in a logic family obey the static discipline when used with other gates in the family.

1.6 CMOS Transistors

Transistors: Electrically controlled switches that turn on or off when a voltage or current is applied to a control terminal. There are two main type of transistors:


- bipolar junction transistors
- metal-oxide-semiconductor field effect transistors (MOSFETs or MOS transistors)

Semiconductors: MOS transistors are built from silicon. The conductivity of silicon changes over many orders of magnitude depending on the concentration of dopants (impurities in the silicon lattice). Adding a dopant with more electrons than the silicon can bind to creates a negative charge which can move around the lattice and is called an n-type dopant. Adding a dopant with less electrons creates a positive charge and hence called a p-type dopant.

Diodes: Junction between p-type and n-type silicon. The p-type region is called the anode and the n-type region called the cathode. When voltage on the anode rises above the voltage on the cathode, the diode is forward biased, and current flows through the diode from the anode to the cathode otherwise it is reverse biased and no current flows.

Capacitors: Consists of two conductors separated by an insulator. When a voltage V is applied to one of the conductors, the conductor accumulates electric charge and the other conductor accumulates the opposite charge $-Q$. The capacitance C of the capacitor is the ratio of charge to voltage $C = \frac{Q}{V}$. More capacitance means that a circuit will be slower and require more energy to operate (charging and discharging takes time).

nMOS and pMOS Transistors: n-type transistors called nMOS, have regions of n-type dopants adjacent to the gate and built on a p-type semiconductor substrate. pMOS transistors are the opposite. Chips which have both nMOS and pMOS transistors are called complementary MOS or CMOS.

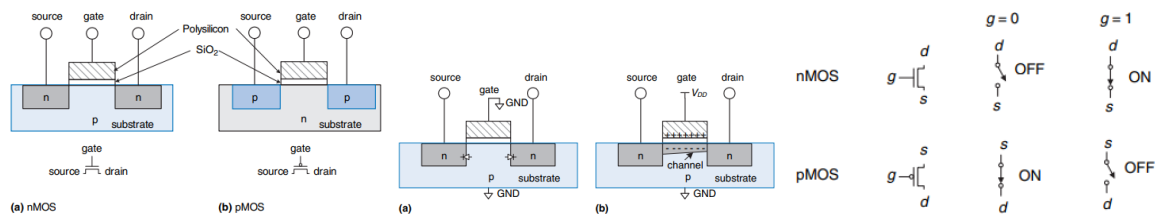

Chapter 2

Combinational Logic Design

2.1 Basic Definitions:

functional specification: Describes the relationship between inputs and outputs

timing specification: Describes the delay between inputs changing and outputs responding

combinational circuit: The output depends only on the current values of the inputs. (e.g a logic gate) A combinational circuit is memoryless.

sequential circuit: The output depends on both current and previous values of the inputs. Sequential circuits have memory.

Bus: A bundle of multiple signals. A single line with a slash through it and a number next to it indicates a bus with the number specifying the number of signals

Combinational composition: A circuit is combinational if:

- Every circuit element itself is combinational
- Every node(wire) of the circuit is either designated as an input to the circuit or connects to exactly one output terminal of a circuit element.
- The circuit contains no cyclic paths: every path through the circuit visits each circuit node at most once.

2.2 Boolean Equations

complement: The complement of a variable/literal A is its inverse \overline{A}

product/implicant: The AND of one or more literals

minterm: A product involving all of the inputs to the function

sum: The OR of one or more literals

maxterm: A sum involving all the inputs to the function

order of operations: NOT has the highest precedence followed by AND then OR

Sum of Products Form: Given a truth table we can create a boolean equation by summing each of the minterms for which the output Y is TRUE.

Product of Sums Form: We can write a boolean equation for any circuit directly from the truth table as the AND of each of the maxterms for which the output is FALSE.

2.3 Boolean Algebra

Table 2.1 Axioms of Boolean algebra

| Axiom | Dual | Name |
|------------------------------------|---------------------------|--------------|
| A1 $B = 0$ if $B \neq 1$ | A1' $B = 1$ if $B \neq 0$ | Binary field |
| A2 $\overline{0} = 1$ | A2' $\overline{1} = 0$ | NOT |
| A3 $0 \bullet 0 = 0$ | A3' $1 + 1 = 1$ | AND/OR |
| A4 $1 \bullet 1 = 1$ | A4' $0 + 0 = 0$ | AND/OR |
| A5 $0 \bullet 1 = 1 \bullet 0 = 0$ | A5' $1 + 0 = 0 + 1 = 1$ | AND/OR |

Table 2.2 Boolean theorems of one variable

| Theorem | Dual | Name |
|----------------------------------|----------------------------|--------------|
| T1 $B \bullet 1 = B$ | T1' $B + 0 = B$ | Identity |
| T2 $B \bullet 0 = 0$ | T2' $B + 1 = 1$ | Null Element |
| T3 $B \bullet B = B$ | T3' $B + B = B$ | Idempotency |
| T4 $\overline{\overline{B}} = B$ | | Involution |
| T5 $B \bullet \overline{B} = 0$ | T5' $B + \overline{B} = 1$ | Complements |

Table 2.3 Boolean theorems of several variables

| Theorem | Dual | Name |
|---|--|---------------------|
| T6 $B \bullet C = C \bullet B$ | T6' $B + C = C + B$ | Commutativity |
| T7 $(B \bullet C) \bullet D = B \bullet (C \bullet D)$ | T7' $(B + C) + D = B + (C + D)$ | Associativity |
| T8 $(B \bullet C) + (B \bullet D) = B \bullet (C + D)$ | T8' $(B + C) \bullet (B + D) = B + (C \bullet D)$ | Distributivity |
| T9 $B \bullet (B + C) = B$ | T9' $B + (B \bullet C) = B$ | Covering |
| T10 $(B \bullet C) + (B \bullet \overline{C}) = B$ | T10' $(B + C) \bullet (B + \overline{C}) = B$ | Combining |
| T11 $(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D) = B \bullet C + \overline{B} \bullet D$ | T11' $(B + C) \bullet (\overline{B} + D) \bullet (C + D) = (B + C) \bullet (\overline{B} + D)$ | Consensus |
| T12 $\overline{B_0 \bullet B_1 \bullet B_2 \dots} = (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$ | T12' $\overline{B_0 + B_1 + B_2 \dots} = (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots)$ | De Morgan's Theorem |

Rules for bubble pushing:

- Pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa.
- Pushing a bubble from the output back to the inputs puts bubbles on all gate inputs
- Pushing bubbles on all gate inputs forward toward the output puts a bubble on the output
- Begin at the output of the circuit and work toward the inputs
- Push any bubbles on the final output back toward the inputs so that you can read an equation in terms of the output instead of the complement of the output
- Working backward, draw each gate in a form so that bubbles cancel. If the current gate has an input bubble, draw the preceding gate with an output bubble. If the current gate does not have an input bubble draw the preceding gate without an output bubble

2.4 From Logic to Gates

schematic: A diagram of a digital circuit showing the elements and the wires that connect them together. The guidelines for drawing schematics:

- Inputs are on the left (or top) side of a schematic
- Outputs are on the right (or bottom) side of a schematic
- Whenever possible, gates should flow from left to right
- Straight wires are better to use than wires with multiple corners
- Wires always connect as a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing without a dot make no connection

Dont Cares: The symbol X is used to describe inputs that the output doesn't care about. When creating a boolean equation from a truth table with dont cares we can use the sum of products and ignore inputs with X's.

2.5 Multilevel Combinational Logic:


two-level logic: Logic in sum-of-products because it consists of literals connected to a level of AND gates connected to a level of OR gates. Circuits with more than two levels of logic may use less hardware.

2.6 X's and Z's

Illegal Value: X The symbol X indicates that the circuit node has an unknown or illegal value. This happens if it is being driven to both 0 and 1 at the same time. This situation is called **contention** and is considered an error and must be avoided. The voltage at contention is usually in the forbidden zone. In a truth table X is defined as "dont care" i.e it is unimportant if it is a 0 or a 1.

Floating Value: Z This symbol indicates that a node is being driven neither HIGH nor LOW. A floating node does not always mean there is an error in the circuit, so long as some other circuit element drives the node to a valid logic level when its value is relevant

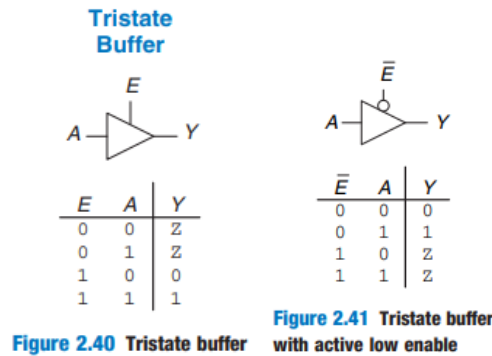Tristate Buffer: Commonly used on busses that connect multiple chips. Only one chip at a time is allowed to assert its enable signal to drive a value onto the busses.




2.7 Karnaugh Maps

Karnaugh maps (K-maps) A graphical method for simplifying Boolean equations. Each square in the K-map corresponds to a row in the truth table and contains the value of the output Y for that row (each square represents a single minterm). The combinations of the row are in gray code (00,01,11,10) which ensures entries differ only in a single variable. The K-map wraps around i.e squares on the far right are effectively adjacent to the squares on the far left.

Logic Minimization with K-Maps: We can minimize logic by circling all the rectangular blocks of 1's in the map, using the fewest number of circles. Each circle should be as large as possible. Then read off the implicants that were circled. Rules for finding a minimized equation from a K-map are as follows:

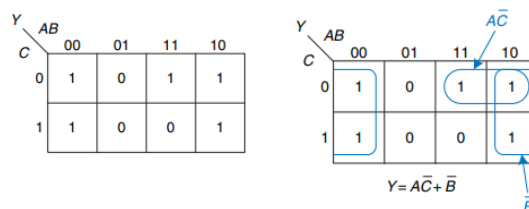
- use the fewest circles necessary to cover all the 1's
- all the squares in each circle must contain 1's
- Each circle must span a rectangular block that is a power of 2
- each circle should be as large as possible
- a circle may wrap around the edges of the K-map
- A 1 in a K-map may be circled multiple times if doing so allows fewer circles to be used




Dont Cares: Dont cares also appear in truth table outputs where the output value is unimportant or the corresponding input combination can never happen. Such outputs can be treated as either 0's or 1's at the designers discretion. In a K-map they can be circled if they help cover the 1's with fewer or larger circles.

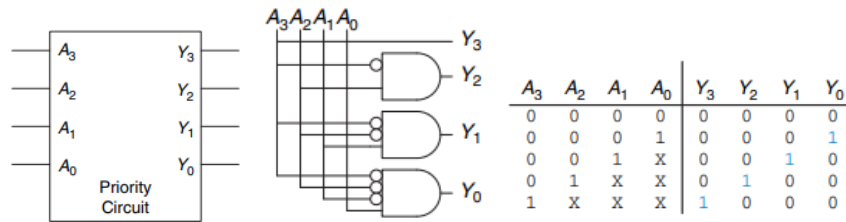2.8 Combinational Building Blocks:

Priority Circuit: Output with the highest priority signal becomes 1 the rest 0.



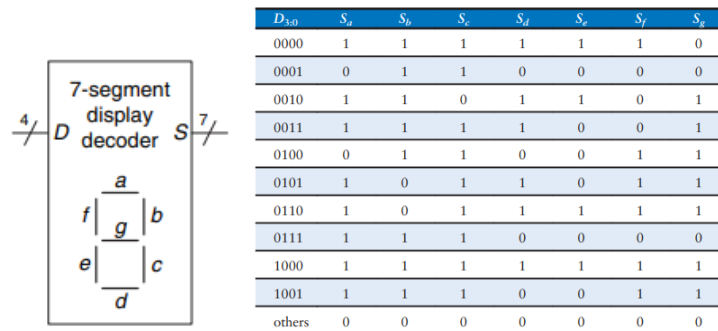Seven Segment Display Decoder: Takes a 4-bit data input $D_{3:0}$ and produces seven outputs to control light emitting diodes to display a digit from 0 to 9.



Multiplexers: Chooses an output from several possible inputs based on the value of a select signal. (Multiplexer is also called a mux) An $N:1$ multiplexer needs $\log_2 N$ select lines. A 2^N -input multiplexer can be programmed to perform any N -input logic function by applying 0's and 1's to the appropriate data inputs.


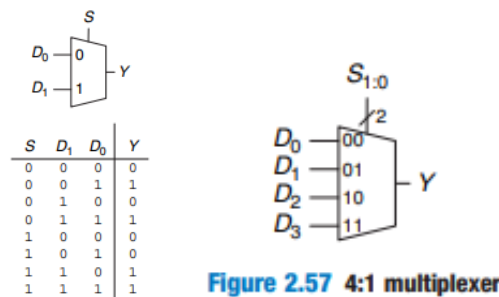


Figure 2.57 4:1 multiplexer

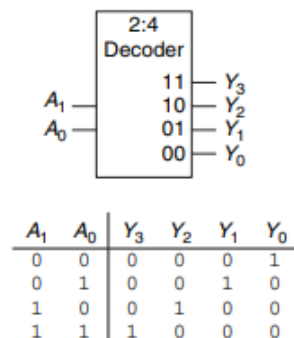Decoder: A decoder has N inputs and 2^N outputs. It asserts exactly one of its outputs depending on the input combination. An N -input function with M 1's in the truth table can be built with an $N : 2^N$ decoder and an M -input OR gate attached to all of the minterms containing 1's in the truth table.




2.9 Timing

delay: The time it takes the output to change in response to an input change. Delay is measured from the 50% point of the input signal to the 50% point of the output signal

rising/falling edge: The transition from LOW to HIGH (rising) and HIGH to LOW (falling).

propagation delay: denoted t_{pd} is the maximum time from when an input changes until the output or outputs reach their final value. It is the sum of the propagation delays through each element on the critical path.

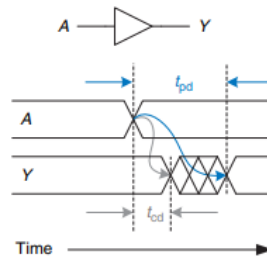contamination delay: denoted t_{cd} is the minimum time from when an input changes until any output starts to change its value. The sum of contamination delays through each element on the short path.



Critical path: The longest and slowest path in a circuit. The path is critical because it limits the speed at which the circuit operates.

Short path: The shortest and therefore the fastest path through the circuit.

Glitches\Hazards : A single input transition which causes multiple output transitions. In a K-map the transition across the boundary of two prime implicants(bubbles) indicates a possible glitch. To fix this we add another circle that covers that prime implicant boundary

Chapter 3

Sequential Logic Design


State: The state of a digital sequential circuit is a set of bits called state variables that contain all the information about the past necessary to explain the future behavior of the circuit. An element with N stable states conveys $\log_2 N$ bits of information (a bistable element stores one bit)

3.1 Latches and Flip-Flops


bistable: An element with two stable states

cross-coupled: The input of one element is the output of the other element and vice versa

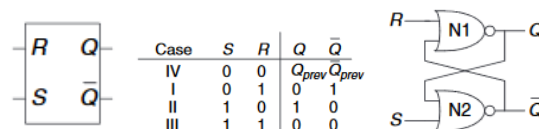
SR-Latch: Consists of two cross-coupled NOR gates. The latch has two inputs, S (set) and R (reset). Setting a bit means to make it TRUE. To reset a bit means to make it FALSE.



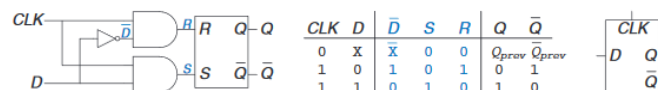
D Latch: Consists of two inputs. The data input D, controls what the next state should be. The clock input CLK controls when the state should change. When $CLK = 1$ the latch is transparent the data at D flows through to Q as if the latch were just a buffer. When $CLK = 0$, the latch is opaque, it blocks new data from flowing through to Q, and Q retains the old value




D Flip-Flop: Is built from two back to back D latches controlled by complementary clocks. The first latch L1 is called the master. The second latch L2, is called the slave. The node between them is named N1. When the \bar{Q} is not needed the condensed symbol is used. The D flip flop copies D to Q on the rising edge of the clock, and remembers its state at all other times. Triangle in the symbols denotes an edge-triggered clock input.

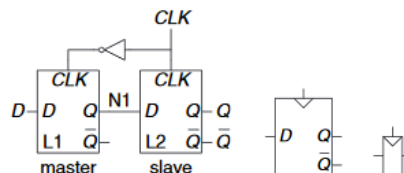

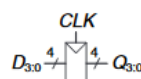
Register: An N-bit register is a bank of N flip-flops that share a common CLK input, so that all bits of the register are updated at the same time.



Enabled Flip-Flop: An enabled flip-flop adds another input EN to determine whether data is loaded on the clock edge. When EN is TRUE the enabled flip-flop behaves like an ordinary D flip-flop. When EN is FALSE the enabled flip-flop ignores the clock and retains its state. Enabled flip flops are useful when we wish to load a new value into a flip flop only some of the time, rather than on every clock edge.

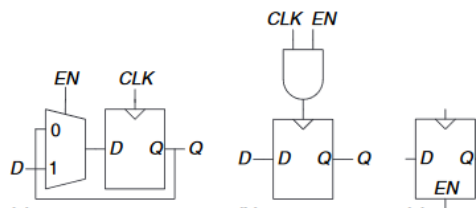

Resettable Flip-flop: A resettable flip flop adds another input called RESET. When RESET is FALSE it behaves like an ordinary D flip-flop. When RESET is TRUE the resettable flip-flop ignores D and resets the output to 0. Resettable flip-flops are useful when we want to force a known state (i.e 0) into all the flip flops in a system when we first turn it on. They can be synchronously (reset themselves only on the rising edge of CLK) or asynchronously resettable (reset as soon as RESET becomes TRUE, independent of CLK). Active low signal means that the reset signal performs its function when it is 0, not 1.

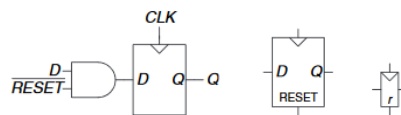

3.2 Synchronous Logic Design

cyclic paths: Outputs are fed directly back to inputs. These circuits are sequential (Combinational logic has no cyclic paths and no races)

synchronized: The state of a system only changes at clock edge

sequential circuit: A circuit with a finite set of discrete states $\{S_0, S_1, \dots, S_{k-1}\}$

synchronous sequential circuit: A sequential circuit which has a clock input whose rising edge indicate a sequence of times at which state transitions occur. The timing specification consists of an upper bound t_{pcq} and a lower bound t_{ccq} on the time from the rising edge of the clock until the output changes, as well as setup and hold times t_{setup}, t_{hold} which indicate when the inputs must be stable relative to the rising edge of the clock. A circuit is a synchronous sequential circuit if:

- Every circuit element is either a register or a combinational circuit
- At least one circuit element is a register
- All registers receive the same clock signal
- Every cyclic path contains at least one register


Sequential circuits that are not synchronous are called **asynchronous**. Current state variable is denoted S and the next state variable S'.

3.3 Finite State Machines(FMS)

FSM's: A circuit with k registers can be in one of 2^k unique states. An FSM has M inputs, N outputs and k bits of state. It also receives a clock and optionally a reset signal. An FSM consists of two blocks of combinational logic, next state logic and output logic and a register that stores the state. On each clock edge the FSM advances to the next state, which was computed based on the current state and inputs.

Moore Machines: FSM where the outputs depend only on the current state of the machine. (a)

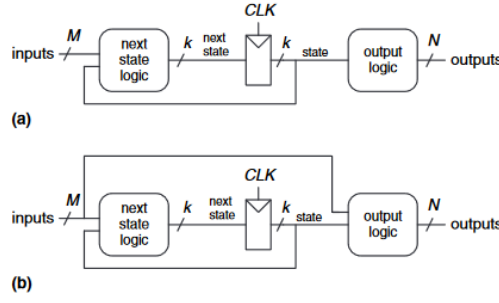Mealy Machines: FSM where the output depends on both the current state and the current inputs (b)



State Transition diagram: Indicates all the possible states of a system and the transitions between these states. Circles represent states and arcs represent transitions between states. The transitions take place on the rising edge of the clock and is not shown in the diagram because a clock is always present in a synchronous sequential circuit. The arcs are labeled with input indicating how it reaches the next state. The value that the outputs have while in a particular state are indicated in the state.

State Transition Table: Indicates for each state and input what the next state should be. The table uses don't care symbols (X) whenever the next state does not depend on a particular input. Reset is omitted from the table. The states and outputs must be assigned binary encodings

Output Table: Indicates for each state what the output should be in that state

Example: Traffic Light: Given inputs T_A, T_B (sensors detecting when people are present) and outputs L_A, L_B (Traffic lights) create the State Machine circuit.

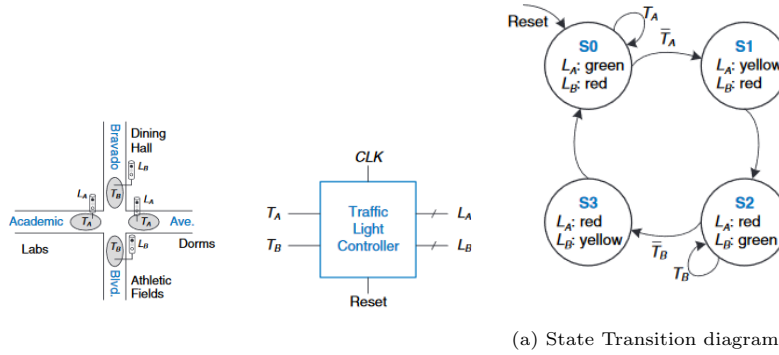


Table 3.1 State transition table

| Current State S | Inputs T_A, T_B | | Next State S' |
|-------------------|-------------------|---|-----------------|
| S0 | 0 | X | S1 |
| S0 | 1 | X | S0 |
| S1 | X | X | S2 |
| S2 | X | 0 | S3 |
| S2 | X | 1 | S2 |
| S3 | X | X | S0 |

Table 3.2 State encoding

| State | Encoding S_{i0} |
|-------|-------------------|
| S0 | 00 |
| S1 | 01 |
| S2 | 10 |
| S3 | 11 |

Table 3.3 Output encoding

| Output | Encoding L_{i0} |
|--------|-------------------|
| green | 00 |
| yellow | 01 |
| red | 10 |

Table 3.4 State transition table with binary encodings

| Current State S_1, S_0 | Inputs T_A, T_B | | Next State S'_1, S'_0 | |
|--------------------------|-------------------|---|-------------------------|---|
| 0 0 | 0 | X | 0 | 1 |
| 0 0 | 1 | X | 0 | 0 |
| 0 1 | X | X | 1 | 0 |
| 1 0 | X | 0 | 1 | 1 |
| 1 0 | X | 1 | 1 | 0 |
| 1 1 | X | X | 0 | 0 |

Table 3.5 Output table

| Current State S_1, S_0 | | Outputs $L_{A1}, L_{A0}, L_{B1}, L_{B0}$ | | | |
|--------------------------|---|--|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 |

From the state transition table and output table we can get the boolean equations needed for the next states and outputs.

- $S'_1 = S_1 \oplus S_0$
- $S'_0 = \bar{S}_1 \bar{S}_0 \bar{T}_A + S_1 \bar{S}_0 \bar{T}_B$
- $L_{A1} = S_1$
- $L_{A0} = \bar{S}_1 S_0$
- $L_{B1} = \bar{S}_1$
- $L_{B0} = S_1 S_0$

Using these formulas we can build the next state logic and the output logic and hence the complete circuit.

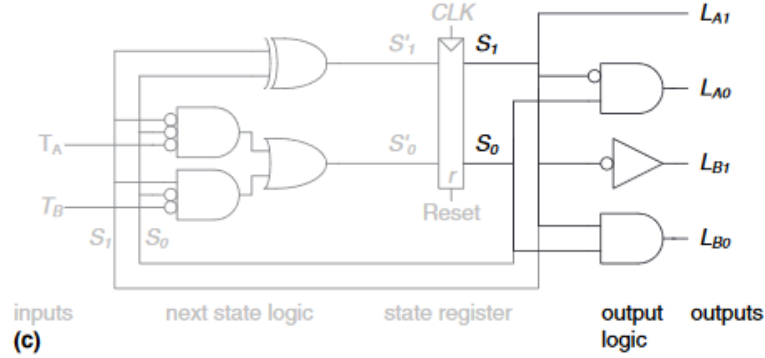


Figure 3.26 State machine circuit for traffic light controller

Binary encoding: Each state is represented as a binary number. A system with K states only need $\log_2 K$ bits of state

One-hot encoding: A separate bit of state is used for each state. Only one bit is "hot" (TRUE) at any time. This encoding requires more flip flops than binary encoding, however the next-state and output logic is often simpler so fewer gates are required. The best encoding choice depends on the specific FSM.